



ASSIGNMENT 1

[Design a UP/DOWN DECADE COUNTER
using J-K flip flops]

NAME: ROHIT SADHU

ROLL NO.: 002010501074

Experiment Name :

Page No.

Objective:- To design a UP/Down decade counter using J-K flip flops

Theory:- A decade counter is a sequential circuit that counts from 0 to 9 and returns back to 0 from 9.


No. of states = 10.

Range = 0 to 9.

No. of flip flops required = 4.

We use a control line to control if the counter is UP or Down. When it is 0 the counter is UP and when it is 1 the counter is Down.

State Diagram:-

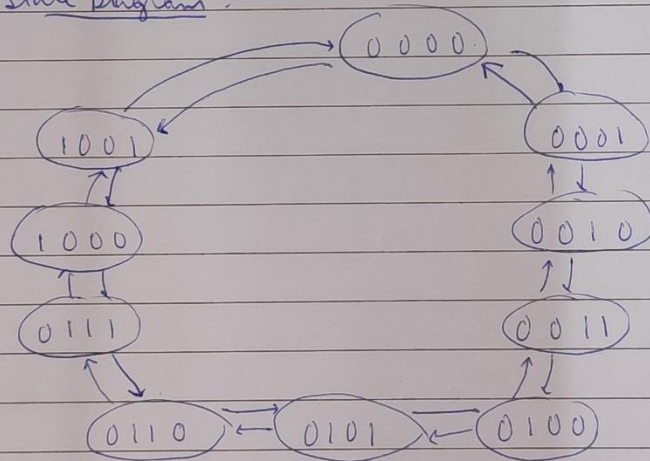

Onward

Teacher's Signature & Date :

Experiment Name :

Page No.

Excitation Table for JK FlipFlop:-

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Discrete Excitation Table:-

CL	Present				Next				F-F							
M	Q_A	Q_B	Q_C	Q_D	Q_{A+1}	Q_{B+1}	Q_{C+1}	Q_{D+1}	J_A	K_A	J_B	K_B	J_C	K_C	J_D	K_D
0	0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
0	1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
0	1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1
1	0	0	0	0	1	0	0	1	1	X	0	X	0	X	1	X
1	0	0	0	1	1	0	0	0	X	0	0	X	0	X	X	1
1	0	0	1	0	0	1	1	1	X	1	X	1	X	1	1	X
1	0	1	1	1	0	1	1	0	0	X	X	0	X	0	X	1
1	0	1	1	0	0	1	0	1	0	X	X	0	X	1	1	X
1	0	1	0	1	0	1	0	0	0	X	X	0	0	X	X	1

Teacher's Signature & Date :

Experiment Name :

Page No.

Cl.	Present				Next				F-F							
M	q_A	q_B	q_C	q_D	q_{A+1}	q_{B+1}	q_{C+1}	q_{D+1}	J_A	K_A	J_B	K_B	J_C	K_C	J_D	K_D
1	0	1	0	0	0	0	1	1	0	x	x	1	1	x	1	x
1	0	0	1	1	0	0	1	0	0	x	0	x	x	0	x	1
1	0	0	1	0	0	0	0	1	0	x	0	x	x	1	1	x
1	0	0	0	1	0	0	0	0	0	x	0	x	0	x	x	1

K-Maps

Map for J_A

$M=0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$M=1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	1	0	0	0
01	0	0	0	0
11	x	x	x	x
10	x	x	x	x

$$J_A = M' q_A' q_B q_C q_D + M q_B' q_C' q_D'$$

Map for K_A

$M=0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	1	x	x

$M=1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	1	0	x	x

$$K_A = M' q_D + M q_D'$$

Teacher's Signature & Date :

Onward

Experiment Name :

Page No.

For J_B :-

$M=0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	0	0	1	0
01	x	x	x	x
11	x	x	x	x
10	0	0	x	x

$M=1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	0	0	0	0
01	x	x	x	x
11	x	x	x	x
10	1	0	x	x

$$J_B = M' q_C q_D + M q_A q_D'$$

For K_B :-

$M=0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	x	x	x	x
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$M=1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	x	x	x	x
01	1	0	0	0
11	x	x	x	x
10	x	x	x	x

$$K_B = M q_C' q_D' + M' q_C q_D$$

Experiment Name :

Page No.

For J_c :-

$M = 0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	0	1	X	X
01	0	1	X	X
11	X	X	X	X
10	0	0	X	X

$M = 1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	0	0	X	X
01	1	0	X	X
11	X	X	X	X
10	1	0	X	X

$$J_c = M q_B q_D' + M q_A q_D' + M' q_A' q_D$$

For K_c

$M = 0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	X	X
10	X	X	X	X

$M = 1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	X	X	0	1
01	X	X	0	1
11	X	X	X	X
10	X	X	X	X

$$K_c = M' q_D + M q_D'$$

For J_D :-

$M = 0$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

$M = 1$

$q_A q_B \backslash q_C q_D$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

$$J_D = 1$$

Onward

Teacher's Signature & Date :

Experiment Name :

Page No.

For K_D :-

$M=0$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	x	1	1	x
01	x	1	1	x
11	x	x	x	x
10	x	1	x	x

$M=1$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	x	1	1	x
01	x	1	1	x
11	x	x	x	x
10	x	1	x	x

$K_D = 1$

Final Expressions:-

$$J_A = M Q_A' Q_C' Q_D' + M' Q_B Q_C Q_D$$

$$\bar{Q}K_A = M Q_D' + M' Q_D$$

$$J_B = M Q_A Q_D' + M' Q_C Q_D$$

$$K_B = M Q_C' Q_D' + M' Q_C Q_D$$

$$J_C = M Q_A Q_D' + M Q_B Q_D' + M' Q_A' Q_D$$

$$K_C = M Q_D' + M' Q_D$$

$$J_D = 1$$

$$K_D = 1$$

Onward™

Teacher's Signature & Date :

CIRCUIT DIAGRAM:

