

Name: Adnan Khurshid

Roll No: 002 010501025

Class: BCSE II

Sem: Second

ASSIGNMENT - 01

Objective: Design an UP-Down (as selected by a central line) Decade counter using JK Flip Flop.

Theory: A decade counter counts from 0 to 9 and returns back to 0 after 9.


No. of states = 10

Range = 0 to 9

No. of flip flops = 4

A control line is used to control if the counter is UP or DOWN. When it is 0, the counter is UP and when it is 1, the counter is DOWN.

State Diagram:

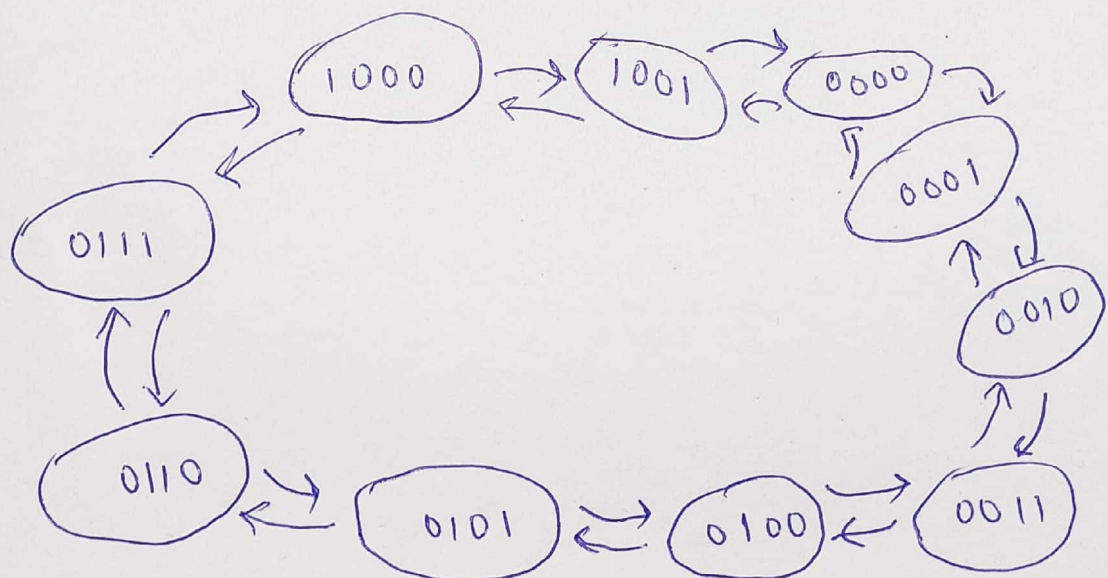

Excitation Table of JK Flip Flop:

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

C.L	Present state				Next state				FlipFlop Inputs							
M	Q _A	Q _B	Q _C	Q _D	Q _{A+1}	Q _{B+1}	Q _{C+1}	Q _{D+1}	J _A	K _A	J _B	K _B	J _C	K _C	J _D	K _D
0	0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	0	1	0	0	1	0	0	x	0	x	0	x	x	1
0	0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	0	1	1	1	1	0	0	0	1	x	x	1	x	1	x	1
0	1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
0	1	0	0	1	0	0	0	0	x	1	0	x	0	x	1	x
1	0	0	0	0	1	0	0	1	1	x	0	x	0	x	x	1
1	1	0	0	1	1	0	0	0	x	0	0	x	0	x	1	x
1	1	0	0	0	0	1	1	1	x	1	1	x	0	x	x	1
1	0	1	1	1	0	1	1	0	0	x	x	0	0	x	1	x
1	0	1	1	0	0	1	0	1	0	x	x	0	0	x	x	1
1	0	1	0	0	0	1	0	0	0	x	x	0	0	x	1	x
1	0	1	0	1	0	0	1	1	0	x	x	1	1	x	1	x
1	0	0	1	1	0	0	1	0	0	x	0	x	x	0	x	1
1	0	0	1	0	0	0	0	1	0	x	0	x	x	1	1	x
1	0	0	0	1	0	0	0	0	0	x	0	x	0	x	x	1

Expressions:

$$J_A = \sum m(7, 16) + d(8, 9, 10, 11, 12, 13, 14, 15, 24, 25, 26, 27, 28, 29, 30, 31)$$

$$K_A = \sum m(9, 24) + d(0, 1, 2, 3, 4, 5, 6, 7, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 26, 27, 28, 29, 30, 31)$$

$$J_B = \sum m(3, 24) + d(4, 5, 6, 7, 10, 11, 12, 13, 14, 15, 20, 21, 22, 23, 26, 27, 28, 29, 30, 31)$$

$$K_B = \sum m(7, 20) + d(0, 1, 2, 3, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 22, 23, 26, 27, 28, 29, 30, 31)$$

$$J_C = \sum m(1, 5, 20, 24) + d(2, 3, 6, 7, 10, 11, 12, 13, 14, 15, 18, 19, 22, 23, 26, 27, 28, 29, 30, 31)$$

$$K_C = \sum m(3, 7, 18, 22) + d(0, 1, 4, 5, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 20, 21, 24, 25, 26, 27, 28, 29, 30, 31)$$

$$J_D = \sum m(0, 2, 4, 6, 8, 16, 18, 20, 22, 24) + d(1, 3, 5, 7, 9, 10, 11, 12, 13, 14, 15, 17, 19, 21, 23, 25, 26, 27, 28, 29, 30, 31)$$

$$K_D = \sum m(1, 3, 5, 7, 9, 17, 19, 21, 23, 25) + d(0, 2, 4, 6, 8, 10, 11, 12, 13, 14, 15, 16, 18, 20, 22, 24, 26, 27, 28, 29, 30, 31)$$

K-Maps

For J_A

when $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

when $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	1	0	0	0
01	0	0	0	0
11	x	x	x	x
10	x	x	x	x

$$J_A = M' Q_B Q_C Q_D + M Q_B' Q_C' Q_D'$$

For K_A

when $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	1	x	x

when $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	1	0	x	x

$$K_A = M' Q_D + M Q_D'$$

For J_B

When $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	X	X

When $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	0	0	0	0
01	X	X	X	X
11	X	X	X	X
10	1	0	X	X

$$J_B = M' Q_C Q_D + M Q_A Q_D'$$

For K_B

When $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	X	X	X	X
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

When $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	X	X	X	X
01	1	0	0	0
11	X	X	X	X
10	X	X	X	X

$$K_B = M Q_C' Q_D' + M' Q_C Q_D$$

For J_c :

When $M=0$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	1	X	X
01	0	1	X	X
11	X	X	X	X
10	0	0	X	X

When $M=1$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	X	X
01	1	0	X	X
11	X	X	X	X
10	1	0	X	X

$$J_c = M Q_B Q_D' + M Q_A Q_D' + M' Q_A' Q_D$$

For K_c

When $M=0$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	X	X
10	X	X	X	X

When $M=1$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	0	1
01	X	X	0	1
11	X	X	X	X
10	X	X	X	X

$$K_c = M' Q_D + M Q_D'$$

For J_D :

when $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

$$J_D = 1$$

when $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

For K_D :

when $M=0$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	X	X	X
10	X	1	X	X

$$K_D = 1$$

when $M=1$

$Q_C Q_D$ $Q_A Q_B$	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	X	X	X
10	X	1	X	X

Final Expressions:

$$J_A = M Q_B' Q_C' Q_D' + M' Q_B Q_C Q_D$$

$$K_A = M Q_D' + M' Q_D$$

$$J_B = M Q_A Q_D' + M' Q_C Q_D$$

$$K_B = M Q_C' Q_D' + M' Q_C Q_D$$

$$J_C = M Q_A Q_D' + M Q_B Q_D' + M' Q_A' Q_D$$

$$K_C = M Q_D' + M' Q_D$$

$$J_D = 1$$

$$K_D = 1$$

